

Lab 2 - The only time you Have to do math

Embedded Systems

Lab Report 2

Anthony Lau


March 7, 2019

Purpose:


In this lab we are going to look at a 4-bit ALU. The first function that we will look at and understand is the ripple carry adder, when can be made from multiple single bit full adders in a structural model in VHDL. Next we will create a 16 function 4-bit ALU behaviorally.

Pre-Lab:

Pre-lab LIVE
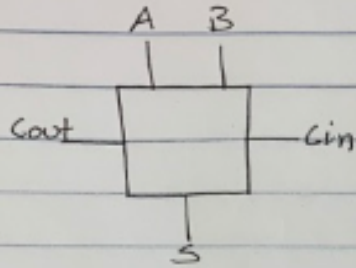
$$Y = A \oplus B \oplus C_{in}$$
$$C_{out} = (A \oplus B)C_{in} + AB$$


A	B	C _{in}	Y	C _{out}
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

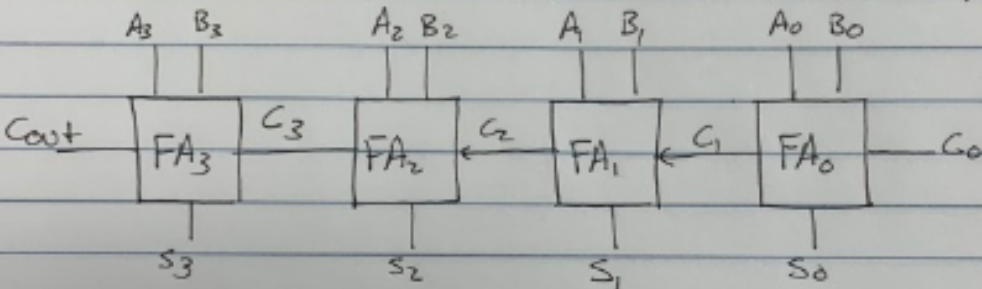

1) Back to Digital Logic Design

Theory:


In this part of the lab we are making a 4-bit ripple carry adder from a 4 single bit full adders. We can construct the truth table for a single bit full adder to write the logic equations for the sum and the carry out. Once we know the equations we can write the VHDL to model the full adder and instantiate it multiple times to create a ripple adder. The ripple adders carry in will be the carry out of the previous full adder.

Truth Table:


A	B	Cin	S	Cout
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Schematic Diagram:

Full Adder

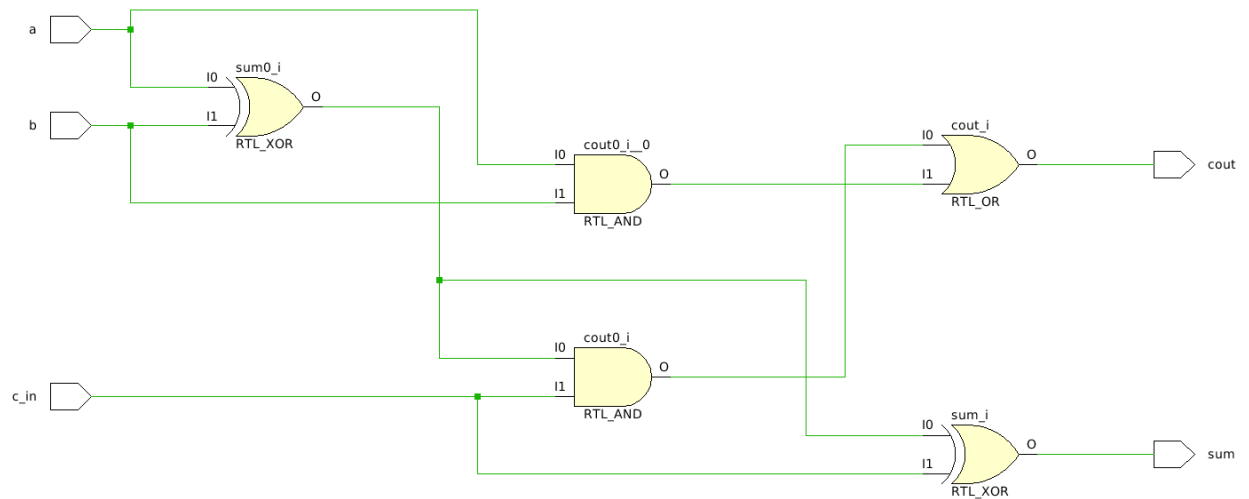

Ripple Adder

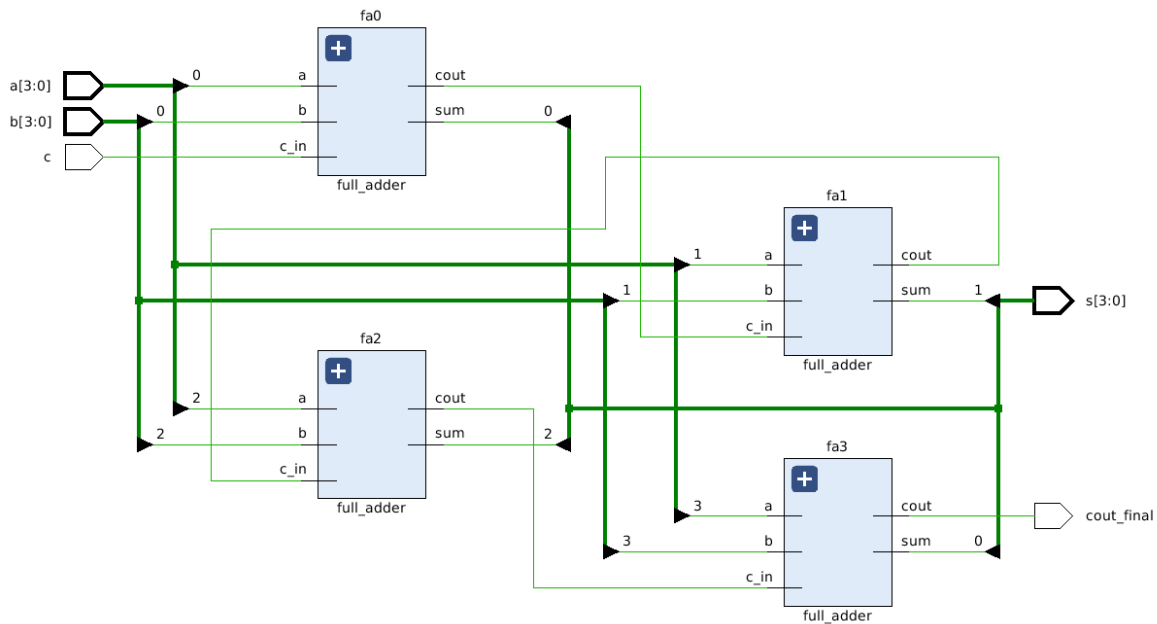

Design:

Full Adder

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity full_adder is
6  Port (a, b, c_in: in std_logic;
7        sum, cout: out std_logic);
8  end full_adder;
9
10 architecture Behavioral of full_adder is
11
12 begin
13
14 sum <= a xor b xor c_in;
15 cout <= ((a xor b) and c_in) or (a and b);
16
17 end Behavioral;

```

Ripple Adder

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4  entity ripple_adder is
5      port(a, b: in std_logic_vector(3 downto 0);

```

```

6         c: in std_logic;
7         s: out std_logic_vector(3 downto 0);
8         cout_final: out std_logic);
9 end ripple_adder;
10
11 architecture four_bit of ripple_adder is
12
13 component full_adder is
14     Port (a, b, c_in: in std_logic;
15           sum, cout: out std_logic);
16 end component;
17
18 signal c1 : std_logic;
19 signal c2 : std_logic;
20 signal c3 : std_logic;
21
22 begin
23 fa0: full_adder
24 port map(a => a(0),
25          b => b(0),
26          c_in => c,
27          sum => s(0),
28          cout => c1);
29
30 fa1: full_adder
31 port map(a => a(1),
32          b => b(1),
33          c_in => c1,
34          sum => s(1),
35          cout => c2);
36
37 fa2: full_adder
38 port map(a => a(2),
39          b => b(2),
40          c_in => c2,
41          sum => s(2),
42          cout => c3);
43
44 fa3: full_adder
45 port map(a => a(3),
46          b => b(3),
47          c_in => c3,
48          sum => s(3),
49          cout => cout_final);
50
51
52 end four_bit;

```

Test:

Testbench


```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.NUMERIC_STD.ALL;
4
5  entity ripple_adder_tb is
6  end ripple_adder_tb;
7
8  architecture testbench of ripple_adder_tb is
9
10     signal tb_a, tb_b: std_logic_vector(3 downto 0);
11     signal tb_sum: std_logic_vector(3 downto 0);
12     signal tb_cout, tb_c: std_logic;
13
14     component ripple_adder is
15         port(a, b: in std_logic_vector(3 downto 0);
16             s: out std_logic_vector(3 downto 0);
17             c: in std_logic;
18             cout_final: out std_logic);
19     end component;
20
21 begin
22
23     generate_inputs: process
24     begin
25         tb_c <= '0';
26         tb_a <= "0000";
27         tb_b <= "0001";
28         wait for 100 ns;
29
30         tb_c <= '0';
31         tb_a <= "0101";
32         tb_b <= "0011";
33         wait for 100 ns;
34
35         tb_c <= '0';
36         tb_a <= "0010";
37         tb_b <= "1000";
38         wait for 100 ns;
39
40         tb_c <= '0';
41         tb_a <= "1100";
42         tb_b <= "0001";
43         wait for 100 ns;
44
45
46         tb_c <= '0';
47         tb_a <= "0110";
48         tb_b <= "0101";
49         wait for 100 ns;
```

```

50
51     tb_c <= '0';
52     tb_a <= "0111";
53     tb_b <= "1010";
54     wait for 100 ns;
55 end process generate_inputs;
56
57 dut: ripple_adder
58 port map(a => tb_a,
59         c => tb_c,
60         b => tb_b,
61         s => tb_sum,
62         cout_final => tb_cout);
63
64 end testbench;

```

Simulation

 


2) Somebody did the work already

Theory:

In VHDL, many basic arithmetic and logical functions are already defined and synthesizable without us having to make our own hardware implementation. For this part we are going to take advantage of that to create a 4-bit 16 function ALU. The ALU will take 3 4-bit inputs A, B and opcode from the switches on the board and perform the operation based on the opcode. The result should be displayed on the leds.

Schematic Diagram:

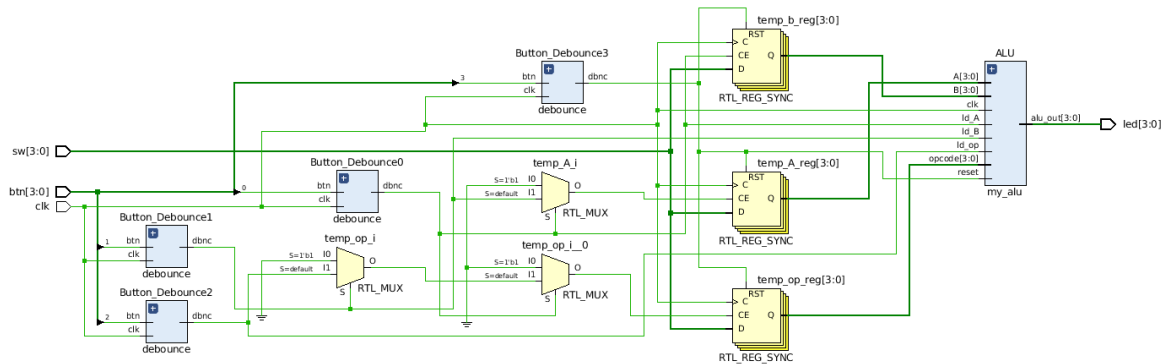

Design:

Debounce

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 entity debounce is
4 Port (clk, btn: in std_logic;
5       dbnc: out std_logic);
6 end debounce;
7
8 architecture Behavioral of debounce is
9
10 signal counter: std_logic_vector(21 downto 0);
11 signal count_set: std_logic;
12 signal shift_register: std_logic_vector(1 downto 0);
13
14 begin
15     process(clk)
16     begin
17         count_set <= shift_register(1) xor shift_register(0);
18         if(rising_edge(clk)) then
19             shift_register(0) <= btn;
20             shift_register(1) <= shift_register(0);
21             if(count_set = '1') then
22                 counter <= (others => '0');
23             elsif(counter(21) = '0') then
```

```

24         counter <= std_logic_vector(unsigned(counter) + 1);
25     else
26         dbnc <= shift_register(1);
27     end if;
28 end if;
29 end process;
30 end Behavioral;

```

My_ALU

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_unsigned.ALL;
4  use IEEE.NUMERIC_STD.ALL;
5
6  entity my_alu is
7  Port (clk, ld_A, ld_B, ld_op, reset: in std_logic;
8        A, B, opcode: in std_logic_vector(3 downto 0);
9        alu_out: out std_logic_vector(3 downto 0));
10 end my_alu;
11
12 architecture Behavioral of my_alu is
13
14 begin
15     process(A, B, opcode, reset)
16     begin
17
18         case(opcode) is
19             when "0000" => alu_out <= A + B;
20             when "0001" => alu_out <= A - B;
21             when "0010" => alu_out <= A + 1;
22             when "0011" => alu_out <= A - 1;
23             when "0100" => alu_out <= 0 - A;
24             when "0101" =>
25                 if(A > B) then
26                     alu_out <= "0001";
27                 else
28                     alu_out <= "0000";
29                 end if;
30             when "0110" => alu_out <= A(2 downto 0) & '0';
31             when "0111" => alu_out <= '0' & A(3 downto 1);
32             when "1000" => alu_out <= A(3) & A(3 downto 1);
33             when "1001" => alu_out <= not A;
34             when "1010" => alu_out <= A and B;
35             when "1011" => alu_out <= A or B;
36             when "1100" => alu_out <= A xor B;
37             when "1101" => alu_out <= A xnor B;
38             when "1110" => alu_out <= A nand B;
39             when "1111" => alu_out <= A nor B;
40         end case;
41     end process;
42 end Behavioral;

```


ALU_Tester

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity alu_tester is
5  Port (btn, sw: in std_logic_vector(3 downto 0);
6        clk: std_logic;
7        led: out std_logic_vector(3 downto 0));
8  end alu_tester;
9
10 architecture Behavioral of alu_tester is
11
12  -----Intermediate Signals-----
13  signal debounced: std_logic_vector(3 downto 0);
14  signal temp_A, temp_b, temp_op, temp_reset: std_logic_vector(3 downto 0);
15
16  -----ALU Component-----
17  component my_alu is
18  Port (clk, ld_A, ld_B, ld_op, reset: in std_logic;
19        A, B, opcode: in std_logic_vector(3 downto 0);
20        alu_out: out std_logic_vector(3 downto 0));
21  end component;
22
23  -----Debounce Component-----
24  component debounce is
25  Port (clk, btn: in std_logic;
26        dbnc: out std_logic);
27  end component;
28
29 begin
30
31    Process(clk)
32    begin
33        if(rising_edge(clk)) then
34            if(debounced(3) = '1') then
35                temp_a <= "0000";
36                temp_b <= "0000";
37                temp_op <= "0000";
38            elsif(debounced(0) = '1') then
39                temp_b <= sw(3 downto 0);
40            elsif(debounced(1) = '1') then
41                temp_a <= sw(3 downto 0);
42            elsif(debounced(2) = '1') then
43                temp_op <= sw(3 downto 0);
44            end if;
45        end if;
46    end process;
47
48
49  Button_Debounce0: debounce
50  port map(clk => clk,
51          btn => btn(0),
```


```

52         dbnc => debounced(0));
53
54 Button_Debounce1: debounce
55 port map(clk => clk,
56         btn => btn(1),
57         dbnc => debounced(1));
58
59 Button_Debounce2: debounce
60 port map(clk => clk,
61         btn => btn(2),
62         dbnc => debounced(2));
63
64 Button_Debounce3: debounce
65 port map(clk => clk,
66         btn => btn(3),
67         dbnc => debounced(3));
68
69 ALU: my_alu
70 port map(clk => clk,
71         ld_A => debounced(0),
72         ld_B => debounced(1),
73         ld_op => debounced(2),
74         reset => debounced(3),
75         A(3 downto 0) => temp_A(3 downto 0),
76         B(3 downto 0) => Temp_B(3 downto 0),
77         opcode(3 downto 0) => Temp_op(3 downto 0),
78         alu_out(3 downto 0) => led(3 downto 0));
79 end Behavioral;


```

Implementation

Elaboration Schematic

 

Synthesis Schematic

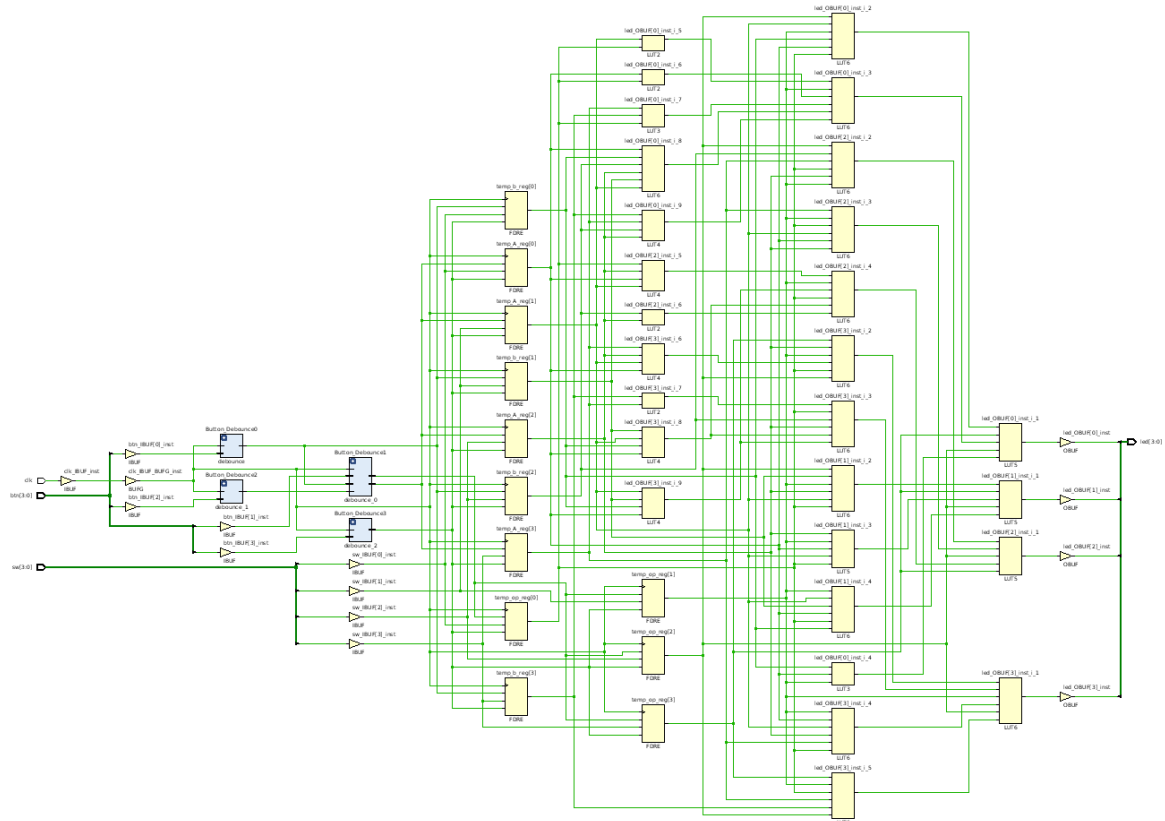

Project Summary


Resource	Utilization	Available	Utilization %
LUT	40	17600	0.23
FF	112	35200	0.32
IO	13	100	13.00
BUFG	1	32	3.13

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.098 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 26.1°C
 Thermal Margin: 58.9°C (5.0 W)
 Effective θ_{JA} : 11.5°C/W
 Power supplied to off-chip devices: 0 W
 Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

XDC File

This file is a general .xdc for the ZYBO Rev B board

To use it in a project:
- uncomment the lines corresponding to used pins
- rename the used signals according to the project

##Clock signal

```
set_property -dict { PACKAGE_PIN L16  IOSTANDARD LVCMOS33 } [get_ports { clk }];  
#IO_L11P_T1_SRCC_35 Sch=sysclk  
create_clock -add -name sys_clk_pin -period 8.00 -waveform {0 4} [get_ports { clk }];
```

##Switches

```
set_property -dict { PACKAGE_PIN G15  IOSTANDARD LVCMOS33 } [get_ports { sw[0] }];  
#IO_L19N_T3_VREF_35 Sch=SW0  
set_property -dict { PACKAGE_PIN P15  IOSTANDARD LVCMOS33 } [get_ports { sw[1] }]; #IO_L24P_T3_34  
Sch=SW1  
set_property -dict { PACKAGE_PIN W13  IOSTANDARD LVCMOS33 } [get_ports { sw[2] }]; #IO_L4N_T0_34  
Sch=SW2  
set_property -dict { PACKAGE_PIN T16  IOSTANDARD LVCMOS33 } [get_ports { sw[3] }];  
#IO_L9P_T1_DQS_34 Sch=SW3
```

##Buttons

```
set_property -dict { PACKAGE_PIN R18  IOSTANDARD LVCMOS33 } [get_ports { btn[0] }]; #IO_L20N_T3_34  
Sch=BTN0  
set_property -dict { PACKAGE_PIN P16  IOSTANDARD LVCMOS33 } [get_ports { btn[1] }]; #IO_L24N_T3_34  
Sch=BTN1  
set_property -dict { PACKAGE_PIN V16  IOSTANDARD LVCMOS33 } [get_ports { btn[2] }]; #IO_L18P_T2_34  
Sch=BTN2  
set_property -dict { PACKAGE_PIN Y16  IOSTANDARD LVCMOS33 } [get_ports { btn[3] }]; #IO_L7P_T1_34  
Sch=BTN3
```

##LEDs

```
set_property -dict { PACKAGE_PIN M14  IOSTANDARD LVCMOS33 } [get_ports { led[0] }]; #IO_L23P_T3_35  
Sch=LED0  
set_property -dict { PACKAGE_PIN M15  IOSTANDARD LVCMOS33 } [get_ports { led[1] }];  
#IO_L23N_T3_35 Sch=LED1  
set_property -dict { PACKAGE_PIN G14  IOSTANDARD LVCMOS33 } [get_ports { led[2] }];  
#IO_0_35=Sch=LED2  
set_property -dict { PACKAGE_PIN D18  IOSTANDARD LVCMOS33 } [get_ports { led[3] }];  
#IO_L3N_T0_DQS_AD1N_35 Sch=LED3
```

In my XDC file I uncommented all the buttons, switches, and leds. I had to rename the port names with the outputs that I have in my VHDL code.

Discussion:

Overall, this lab was not too difficult to figure out. What I learned was that the `std_logic_unsigned` library made it easier to deal with any logic type conversions and allowed me to perform operations directly on the inputs. When there is a negative input, the result shows the two's complement of the negative value. The concepts that I completely understand is how a ripple adder can be made of multiple full adders, and how to implement a 16 function ALU.